

ECE 571- Winter 2020

Homework #1

Create a single .zip or .rar file containing your source code files and transcripts showing that your implementations simulates correctly. Name the file <yourname>_hw1.zip (ex: rkravitz_hw1.zip).

Submit your deliverables to your Homework #1 dropbox no later than 10:00 PM on Sunday 19-Jan-2020. We will only grade the submission with the latest date stamp.


Source code should be structured and commented with meaningful variables. Include a header at the top of each file listing the author and a description. You may use the following template:

```
//////////////////////////////////////////
// <filename>.sv - <one line description>
//
// Author:  <your name> (<your email address>)
// Date:    <date you created the code>
//
// Description:
// -----
// <text description of what function the module performs>
//////////////////////////////////////////
```

Acknowledgement: These problems are based on an exercises from *Advanced Digital Design with the Verilog HDL: 2e* by Michael D. Ciletti, Pearson India Education Services Pvt. Ltd, 2017. Modifications for SystemVerilog designed by Roy Kravitz, 2020.

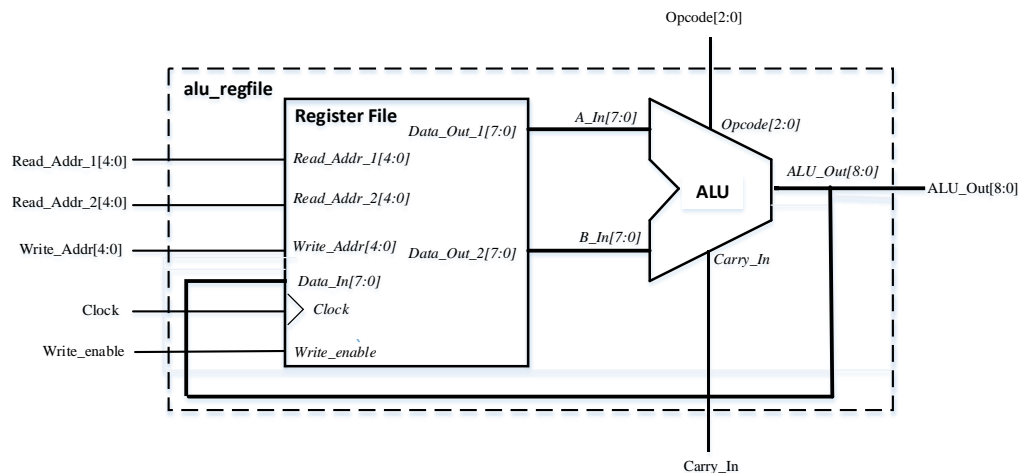Problem 1 (60 pts)

For this homework problem we are going to create a SystemVerilog model for a simple digital system the includes an ALU (Arithmetic Logic Unit) with inputs taken from a 32 entry x 16 bit wide Register File and the results written back to the Register file. A block diagram of the system is shown below:



- A. (25 pts) Write a SystemVerilog module that implements an 8-bit ALU. The ALU is a block of combinational logic that implements the following functionality (ex: Add Opcode = 3'b000,...Exnor Opcode = 3'b111):

Operand	Function
Add	$a + b + c_{in}$
Subtract	$a + \sim b + c_{in}$
Subtract_a	$b + \sim a + \sim c_{in}$
Or_ab	$\{1'b0, a / b\}$
And_ab	$\{1'b0, a \& b\}$
Not_ab	$\{1'b0, (\sim a) \& b\}$
Exor	$\{1'b0, a \wedge b\}$
Exnor	$\{1'b0, a \sim \wedge b\}$

Make use of SystemVerilog constructs as appropriate. The signature for the module is:

```
import ALU_REGFILE_Defs::*;

module alu (
    input logic [ALU_INPUT_WIDTH-1:0] A_In, B_In, // A and B operands
    input logic Carry_In, // Carry In
    input aluop_t Opcode, // operation to perform
    output logic [ALU_OUTPUT_WIDTH-1:0] ALU_Out // ALU result(extended by 1 bit
                                                // to preserve Carry_Out from
                                                // Sum/Diff)
);
```

Note that the ALU Output is one bit wider than the inputs. This is to preserve the Carry Out. Note also the use of a typedef enum for the ALU opcode (operation to perform)

- B. (15 pts) Create a model of the DUT called `alu_regfile` that instantiates instances of your ALU module and the Register File module provided in the release. The signature for the module is:

```
import ALU_REGFILE_Defs::*;

module alu_regfile (

    // register file interface
    input  logic [REGFILE_ADDR_WIDTH-1:0]    Read_Addr_1, // read port addresses
                                              Read_Addr_2,
    input  logic [REGFILE_ADDR_WIDTH-1:0]    Write_Addr,  // write port address
    input  logic                             Write_enable, // write enable (1 to
                                                         // write)
    input  logic [REGFILE_WIDTH-1:0]         Write_data,  // data to write into the
                                                         // register file


    // ALU interface. Data to the ALU comes from the register file
    input  logic                             Carry_In,    // Carry In
    input  aluop_t                           Opcode,      // operation to perform
    output logic [ALU_OUTPUT_WIDTH-1:0]      ALU_Out,     // ALU result

    // system-wide signals
    input  logic                             Clock         // system clock
);
```

- C. (20 pts) Simulate your source code with QuestaSim using the provided testbench to demonstrate that your design is correct. You will be graded on the correctness of your design.

 Question 2 (40 pts)

Write and verify (i.e. write your own testbench) a SystemVerilog model for a “jerky” counter having the sequence shown below:



- A. (15 pts) Write a SystemVerilog model of the counter. Use SystemVerilog constructs as appropriate. The signature for the module is:

```
module jerky_counter (
    input logic      clock, reset,    // clock and reset
    output logic [7:0] count          // counter output
);
```

- B. (15 pts) Write a testbench for your counter. Testbenches for counters are pretty simple. Generate a clock, apply the clock to the counter, and wait a while until the sequence completes. Display the counter output and check your results manually.
- C. (10 pts) Simulate your source code with QuestaSim with your testbench to demonstrate that your design is correct.